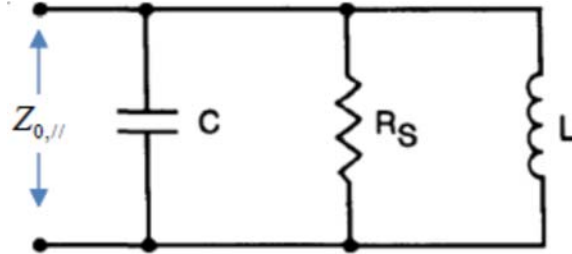


Home Work 17

1. (10 points)




The impedance of a resonator model can be related to a circuit shown above. Show the impedance of above circuit can be expressed as

$$Z_{0, //} = \frac{R_s}{1 + iQ \left(\frac{\omega_R}{\omega} - \frac{\omega}{\omega_R} \right)},$$

and find the expression for Q and ω_R in terms of C , R_s , and L .

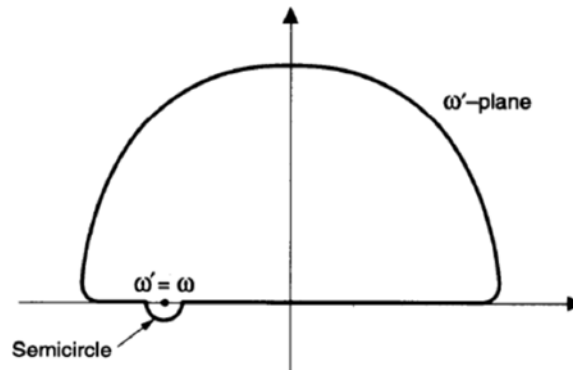2. (10 points) Perform a contour integral of $\frac{Z_{//}(\omega')}{\omega' - \omega}$ in the complex ω' plane over the upper half plane along the contour shown in the figure.



Show that if $Z_{//}(\omega')$ converges sufficiently fast as $|\omega'| \rightarrow \infty$,

$$Z_{//}(\omega) = -\frac{i}{\pi} P.V. \int_{-\infty}^{\infty} \frac{Z_{//}(\omega')}{\omega' - \omega} d\omega', \quad (1)$$

and eq. (1) leads to Kramers-Kronig relations.

$$\operatorname{Re}[Z_{//}(\omega)] = \frac{1}{\pi} P.V. \int_{-\infty}^{\infty} \frac{\operatorname{Im}[Z_{//}(\omega')]}{\omega' - \omega} d\omega'$$
$$\operatorname{Im}[Z_{//}(\omega)] = -\frac{1}{\pi} P.V. \int_{-\infty}^{\infty} \frac{\operatorname{Re}[Z_{//}(\omega')]}{\omega' - \omega} d\omega'$$